

IGBT reverse conduction characteristics

Hard-switching and soft-switching

Energy Saving Products BU
July 2013



International
IOR Rectifier

The IGBT in reverse

The IGBT is a four-layer structure (P-N-P-N). It has a well-defined blocking capability in one direction and a weak and undefined blocking capability in the reverse direction.

The MOSFET is a three-layer structure (N-P-N) with good reverse conduction capabilities.

For more details follow the link below to appnote AN-983, Section 1, [AN-983](#)

IGBTs in topologies with reverse conducting requirements (bridge) need an anti-parallel diode, normally co-packaged with the IGBT. Single-ended topologies (boost PFC) do not require an anti-parallel diode.

A series blocking diode must be added to IGBTs (and FETs) if the topology requires reverse blocking capability (current-fed converters).




Advantages and disadvantages compared to a MOSFET **IR**

The diode co-packaged with the IGBT is targeted to the application.

The MOSFET integral rectifier has a low voltage drop but reverse recovery characteristics are inadequate for high frequency applications.

IR co-packages three different types of diodes targeted to the application:

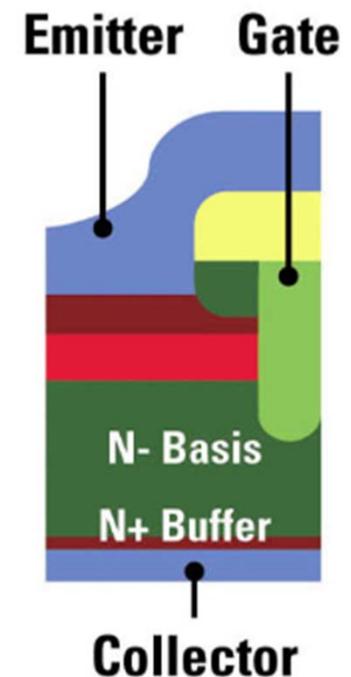- **Very low voltage drop** for resonant and ZVS converters to minimize diode conduction losses
- **Very soft recovery** for motor drives to minimize EMI
- **Very low stored charge** for high frequency applications to minimize recovery and turn-on losses



Soft-switching

The diode co-packaged with the IGBT conducts *before* the IGBT turns on, on account of the resonant nature of the load.

When the IGBT turns on, it has only a diode drop between emitter and collector.

The turn-on losses are virtually zero. See example in next page.

This allows operation at higher frequency.

Application examples: induction heating and some power converters.

Hard-switching

When the IGBT turns on load current is flowing in the antiparallel diode of a *complementary* IGBT.

At turn-on the IGBT picks up the load current plus the reverse recovery current of the diode. See waveform later.

Because of the reverse recovery of the diode turn-on losses are normally higher than turn-off losses.

Most power converters and motor drives operate in this mode.

Soft-switching example





Series Resonant Half-bridge converter (SRHB)

The pink trace is the voltage at the midpoint. The blue trace is the current in a switch.

Diode has no reverse recovery losses because load current transfers from the diode to the antiparallel IGBT with a very low $di/dt < 10A/\mu s$ (ZVS). During the diode reverse recovery load current flows in the IGBT and in the diode (as reverse recovery current). T_{RR} is normally $< 1\mu s$ in these operating conditions

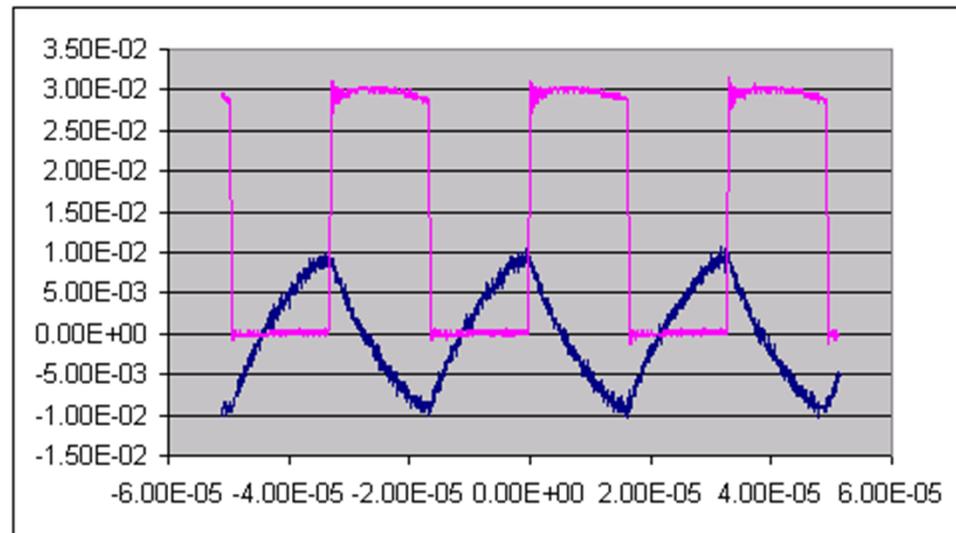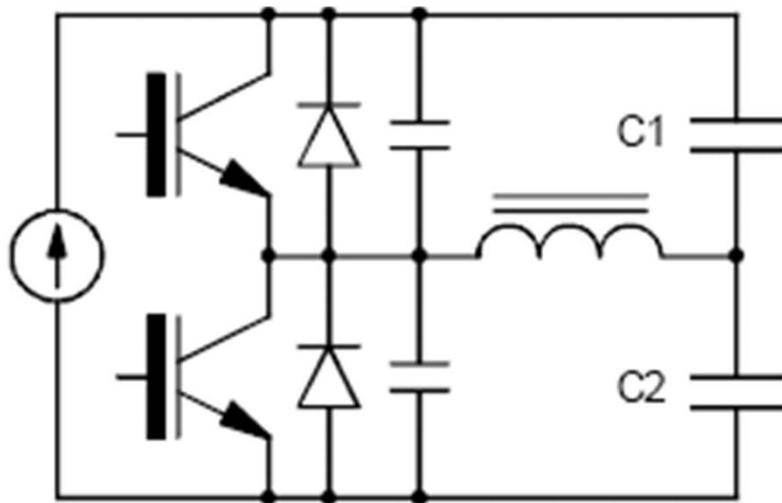
Diode V_{FR} is the important parameter. A large diode V_{FR} increases losses





Hard-switching example



24-Sep-09
14:19:21

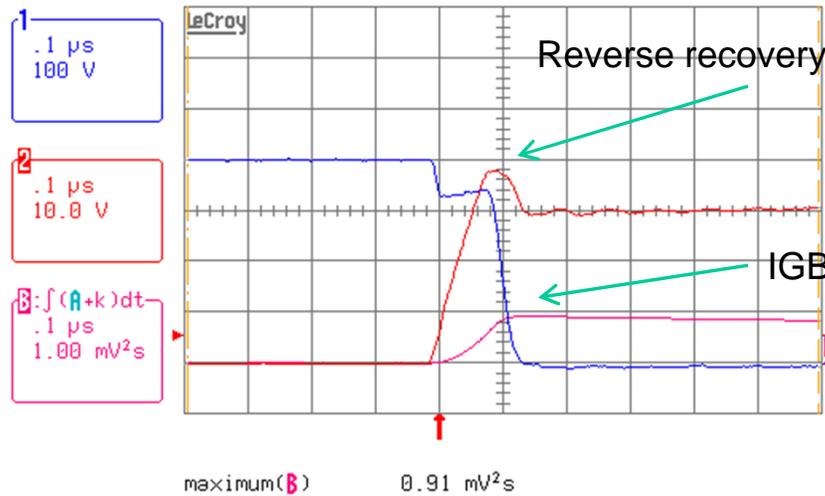

24-Sep-09
14:24:58

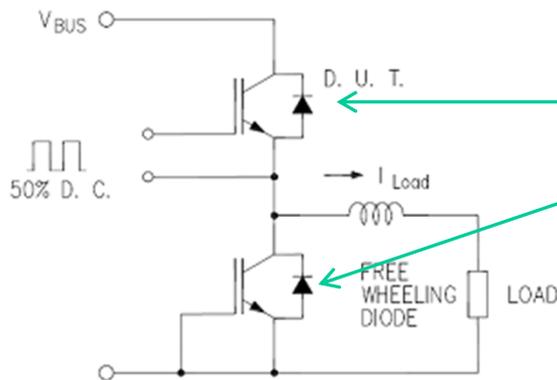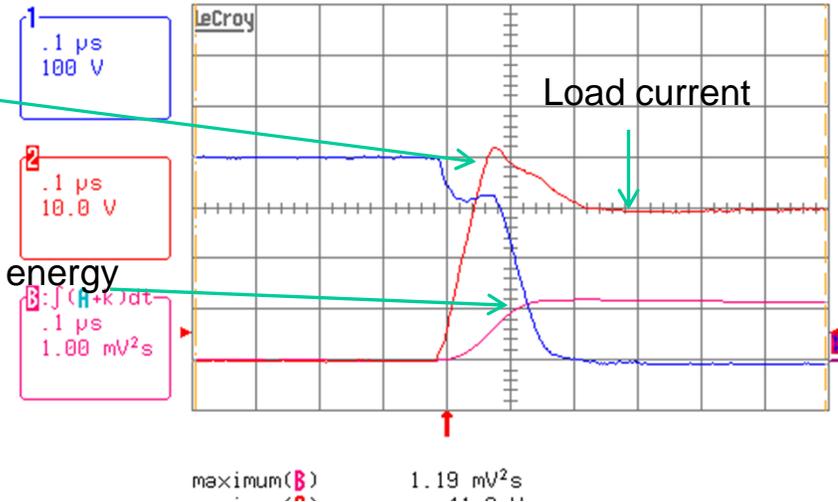

When the D.U.T turns on, load current transfers:

- to IGBT
- from freewheeling diode

Higher reverse recovery charge means higher IGBT turn-on losses


Diode has its own recovery losses, as well. They can be higher or lower than the IGBT turn-on losses, depending on diode and manufacturer.

Soft recovery v. hard recovery



Di/dt during the second half of the reverse recovery measures “softness”

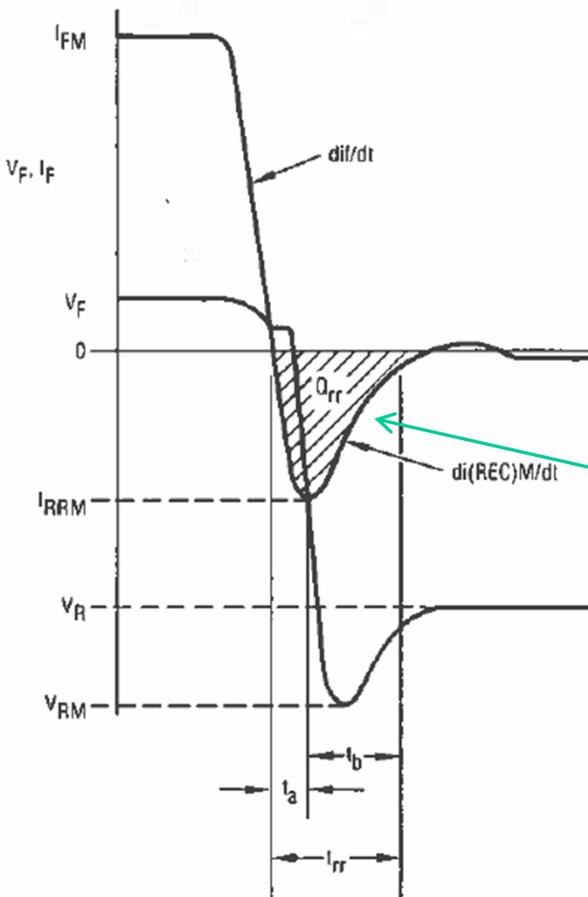A diode with high di/dt is called “snappy”. Frequently this di/dt is the highest di/dt in the circuit. It induces noise in the logic and generates EMI.



Increasing gate drive impedance at turn-on has a small beneficial effect. It normally increases turn-on losses.

Very few manufacturers provide data on “softness”

Di/dt during second half of the reverse recovery