

Simple High Side Drive Provides Fast Switching and Continuous On-Time

By Laszlo Kiraly, International Rectifier

INTRODUCTION

P-channel power MOSFETs are typically used as high-side switches in low power applications because of simpler gate drive circuitry. As power levels, either voltage or current, increase, the advantages of P-channel devices are quickly offset by their increased onresistance, limited voltage range, increased cost, and increased complexity of the gate drive circuitry. By switching to an N-channel device, it is possible to improve on the P-channel's disadvantages, at the expense of increased gate drive complexity. For high power levels, the IGBT is extremely well suited for use as a high-side switch, yet all currently available IGBTs are N-channel devices. Presented is a circuit that, with the use of an extra IC and a few passive components, solves the N-channel gate drive circuit issue.

DEDICATED HIGH SIDE DRIVERS MAKE LIFE EASIER

The Control IC drivers from International Rectifier provide ground referenced, logic level inputs, and high energy, low impedance gate drive for MOSFET or IGBT power transistors up to 500V DC operating voltage when used in switchmode applications. These Control ICs use the bootstrap technique to create gate voltage for the MOS-gated device and to power the floating section of the high-side driver. The advantages of the bootstrap circuit are its simplicity and the fast switching times, but to keep the bootstrap capacitor charged the MOSgated device has to periodically be turned off. With the addition of a simple charge pump, both the fast switching of the bootstrap circuit and unlimited on-time of the charge pump circuit can be achieved.

CIRCUIT AND TEST RESULTS

The schematic diagram of the circuit is shown in Figure 1. The IR2125 ControliC was selected to demonstrate the coop-

eration of the charge pump and the bootstrap circuits. The IR2125 also has an over-current shut down capability, providing protection for the MOS-gated device. To provide the low operating current requirement of the IR2125, the charge pump employs a 555 CMOS timer.

When the IGBT is off, the bootstrap capacitor is charged through the 1 0DF6 diode and the load resistor. When the IGBT is on, the 100 k Ω resistor connected to ground charges the 100 nF capacitor connected between leads 1 and 8 of the 555 timer generating -15V referenced to lead 5 of the IR2125. The charge pump circuit formed by the two 1 N4148 diodes and the 10 nF capacitor which converts the 7.5 kHz square wave at lead 3 of the 555 timer to +15V referenced to Vs and charges the bootstrap capacitor.

Figure 2 shows the circuit waveforms at start-up. As the IGBT turns on, the bootstrap diode disconnects lead 8 of the IR2125 from the +12V power supply, and the voltage across the bootstrap capacitor starts dropping. At the same time the 1 00k resistor located between lead 1 of the 555 timer

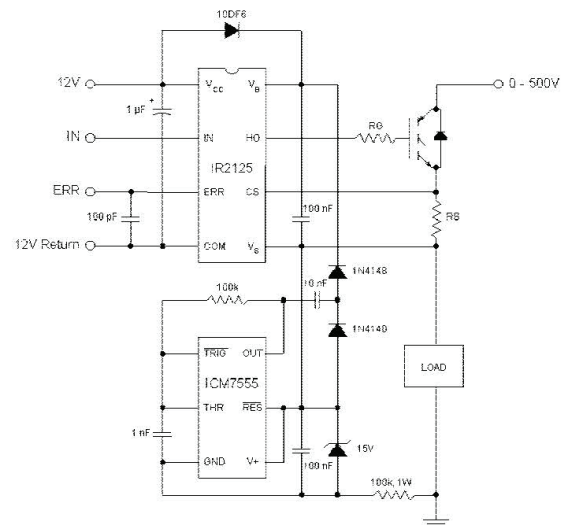


Figure 1
 High side drive provides fast switching, continuous on-time and protection for the switching device

and ground starts charging the 100 nF capacitor connected to it and generates supply voltage for the CMOS (MAXIM ICL715551PA) timer. The output voltage of the charge pump increases with increasing supply voltage. The charge pump maintains the voltage in the bootstrap capacitor, keeping the voltage above the undervoltage threshold level of the IR2125.

This improves system efficiency, expands voltage range, and reduces the cost of the power device required.

DESIGN CONSIDERATIONS

- The absolute maximum voltage supply voltage for the 555 is 18V, consider this when selecting the zener diode and its tolerance.
- The supply current at the V8 pin (I_{SS}) of the IR2125 increases with increasing temperature.
- The 100k 1 kW resistor should be sized according the maximum supply current at the high side of the IR2125, the minimum operating power supply voltage and the timing requirements.

CONCLUSION

This simple, inexpensive charge pump circuit overcomes the maximum on-time limitation of the bootstrap circuit. The circuit presented above utilizes the advantages of the bootstrap and charge pump technique providing excellent switching speed and steady state operation allowing the use of an N-channel MOS-gated power device as a high-side switch.

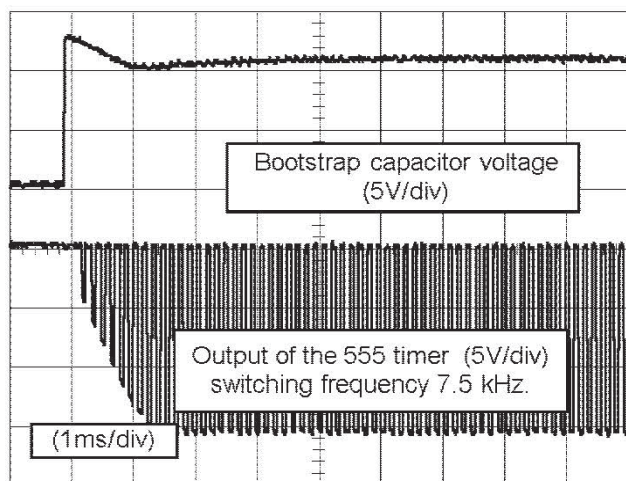


Figure 2